

Derrick Subnaik
Computer Architecture
Homework 1

1.) Fill up the truth table on the right side.

S	X ₀	X ₁	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

2.) Express the Boolean function $Y(S, X_0, X_1)$ with respect to SOP.

$$Y(S, X_0, X_1) = \bar{S}X_0\bar{X}_1 + \bar{S}X_0X_1 + S\bar{X}_0X_1 + SX_0X_1$$

3.) Express the Boolean function $Y(S, X_0, X_1)$ with respect to POS

$$Y(S, X_0, X_1) = (S + X_0 + X_1)(S + X_0 + \bar{X}_1)(\bar{S} + X_0 + X_1)(\bar{S} + \bar{X}_0 + X_1)$$

4.) Using K-map, simplify the boolean function $Y(S, X_0, X_1)$ obtained in (2.)

$$y = SX_1 + \bar{S}X_0$$

S \ X ₀ X ₁	00	01	11	10
0	0	0	1	1
1	0	1	1	0

Annotations: A group of 1s in the top row (S=0) is labeled $\bar{S}X_0$. A group of 1s in the middle column (X₁=1) is labeled SX_1 .


5.) Using K-map, simplify the boolean function $Y(S, x_0, x_1)$ obtained in 3


$S \backslash x_0 x_1$	00	01	11	10
0	0	0	1	1
1	0	1	1	0

$$y = (\bar{S} + x_0)(S + x_1)$$

$$6.) Y(S_0, S_1, X) = \bar{S}_0 \bar{S}_1 Y(0, 0, X) + \bar{S}_0 S_1 Y(0, 1, X) + S_0 \bar{S}_1 Y(1, 0, X) + S_0 S_1 Y(1, 1, X)$$
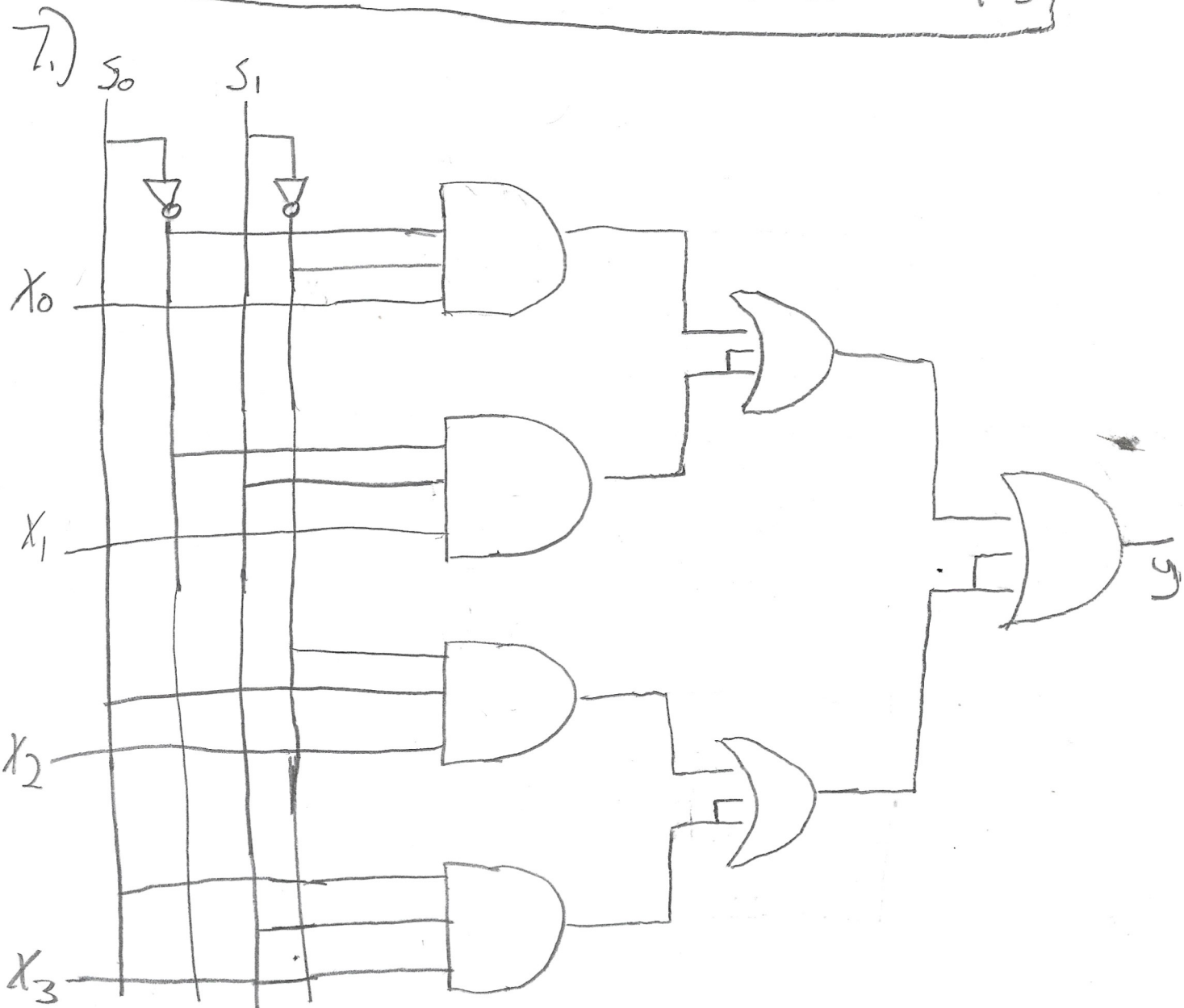
$$Y(S_0, S_1, X) = \bar{S}_0 \bar{S}_1 X_0 + \bar{S}_0 S_1 X_1 + S_0 \bar{S}_1 X_2 + S_0 S_1 X_3$$



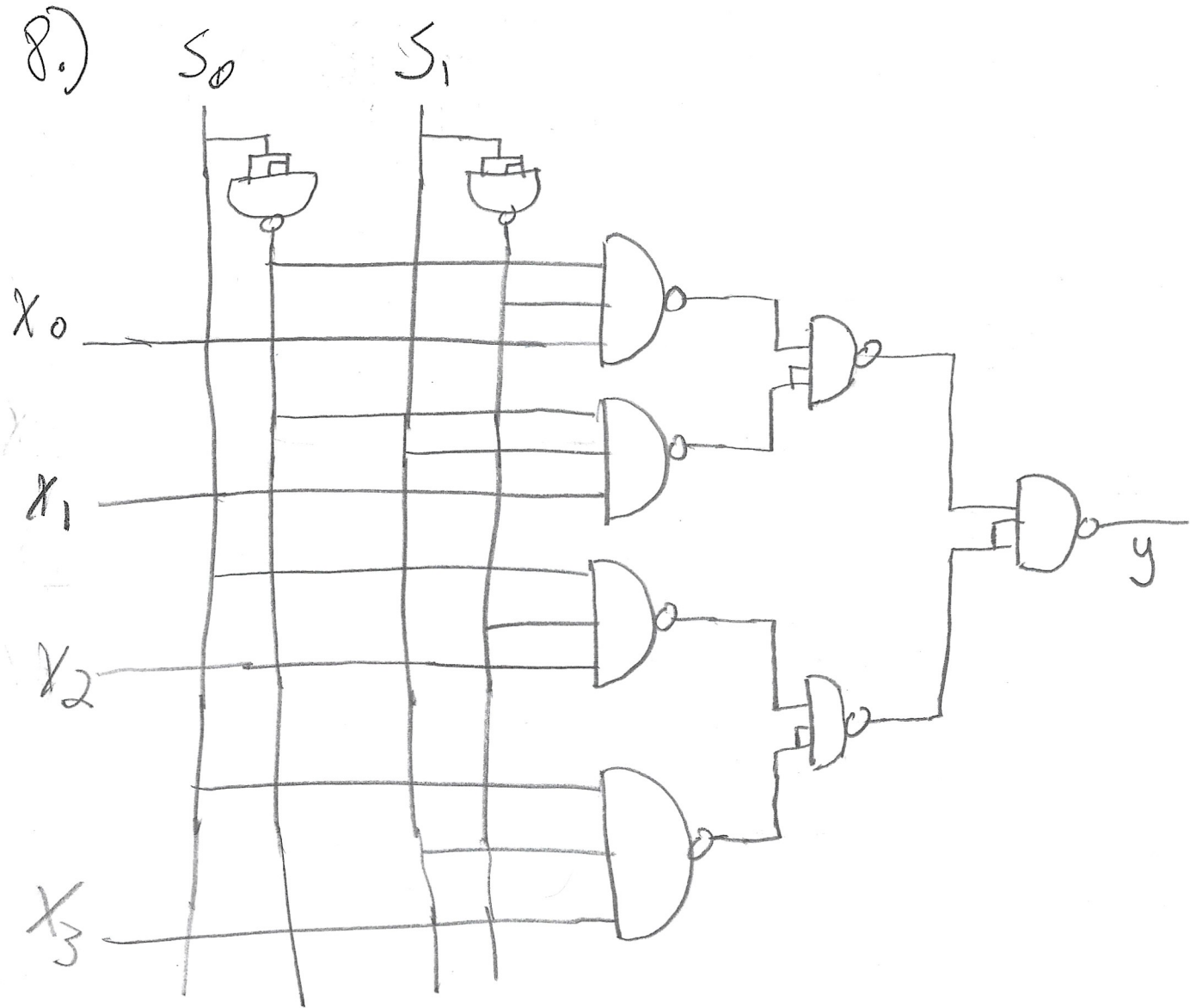

$$Y(S_0, S_1, X) = \underbrace{\bar{S}_0 \bar{S}_1 X_0}_A + \underbrace{\bar{S}_0 S_1 X_1}_B + \underbrace{S_0 \bar{S}_1 X_2}_C + \underbrace{S_0 S_1 X_3}_D$$

$$= \overline{A+B+C+D} = \overline{A} \cdot \overline{B} \cdot \overline{C} \cdot \overline{D}$$

$$Y(S_0, S_1, X) = (\bar{S}_1 \bar{S}_0 X_0) \cdot (\bar{S}_0 S_1 X_1) \cdot (S_0 \bar{S}_1 X_2) \cdot (S_0 S_1 X_3)$$