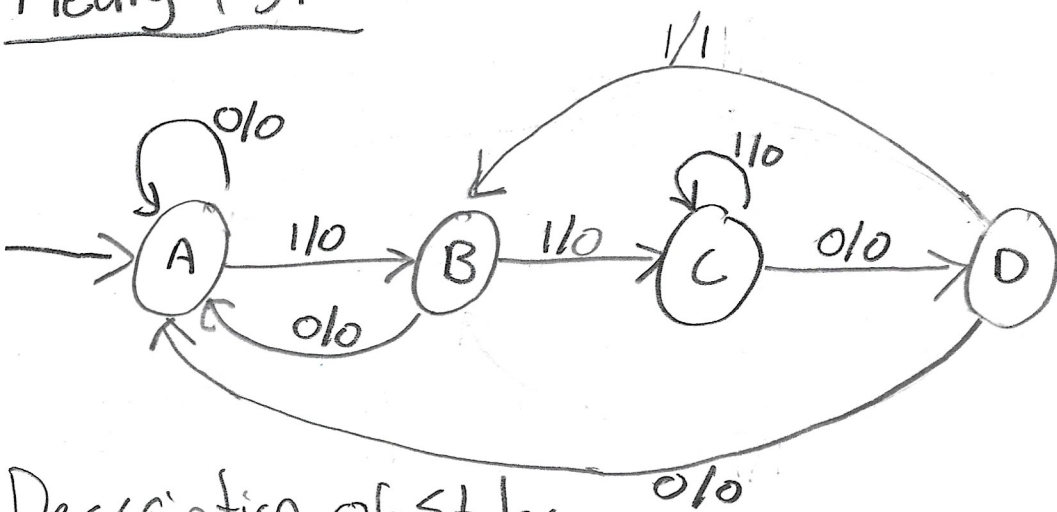


Mealy FSM



Description of States


A: We are waiting 1, that can be the first symbol of 1101

B: We have seen 1, we are now waiting 1, to be the second symbol of 1101

C: We have seen 11, we are now waiting 0, to be the third symbol of 1101

D: We have seen 110, we are now waiting 1, to be the last symbol of 1101

Moore FSM

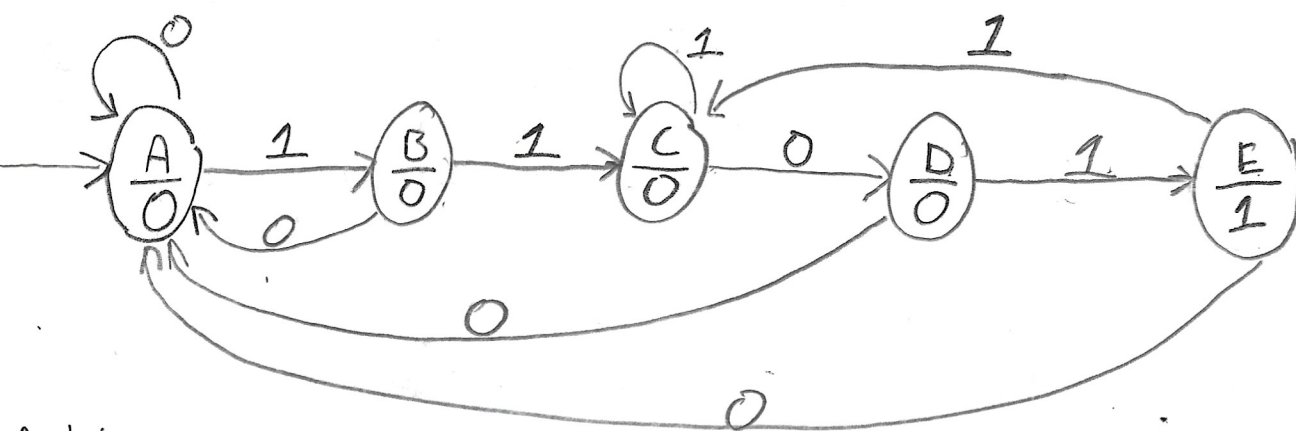

A: We are waiting 1, to be the first symbol of 1101

B: We have seen 1, we are now waiting 1, to be the second symbol of 1101

C: We have seen 11, we are now waiting 0, to be the third symbol of 1101

D: We have seen 110, we are now waiting 1, to be the last symbol of 1101

E: We have seen 1101

Compare FSM's

The Mealy FSM has 4 states, and the Moore FSM has 5 states.

Since the Mealy FSM has 4 states, we can do the state-encoding with 2-bit binary code, the Moore FSM has 5 states we would need 3-bit binary codes. We would need more logic gates for the Moore FSM, which means that the Mealy FSM is more cost-efficient.

State Encoding

	S_1	S_0
A:	0	0
B:	0	1
C:	1	0
D:	1	1

Current state	Input	Next state	Output
A	0	A	0
A	1	B	0
B	0	A	0
B	1	C	0
C	0	D	0
C	1	C	0
D	0	A	0
D	1	B	1

After State Encoding

State-Transition and Output Tables

Current State	Input	Next State	Output
S_1 S_0	I	S_1' S_0'	Y
0 0	0	0 0	0
0 0	1	0 1	0
0 1	0	0 0	0
0 1	1	0 0	0
1 0	0	1 0	0
1 0	1	1 0	0
1 1	0	1 1	0
1 1	1	1 1	1

K-Maps

S_1, S_0		I			
I		00	01	11	10
	0	0	0	0	0
1	0	0	0	1	0

$Y = S_1 S_0 I$

K-Maps

S_1, S_0		I			
I		00	01	11	10
	0	0	0	0	1
1	0	1	0	1	1

$$S_1' = \bar{S}_1 S_0 I + S_1 \bar{S}_0 \text{ or } S_1' = \bar{S}_1 \bar{S}_0 I + S_1 \bar{S}_0 \bar{I} + S_1 S_0 I$$

S_1, S_0		I			
I		00	01	11	10
	0	0	0	0	1
1	1	0	1	1	0

$S_0' = \bar{S}_1 \bar{S}_0 I + S_1 S_0 I + S_1 \bar{S}_0 \bar{I}$

Circuit Schematic

